



DIGITAL LOGIC


数字逻辑



01

Course Content



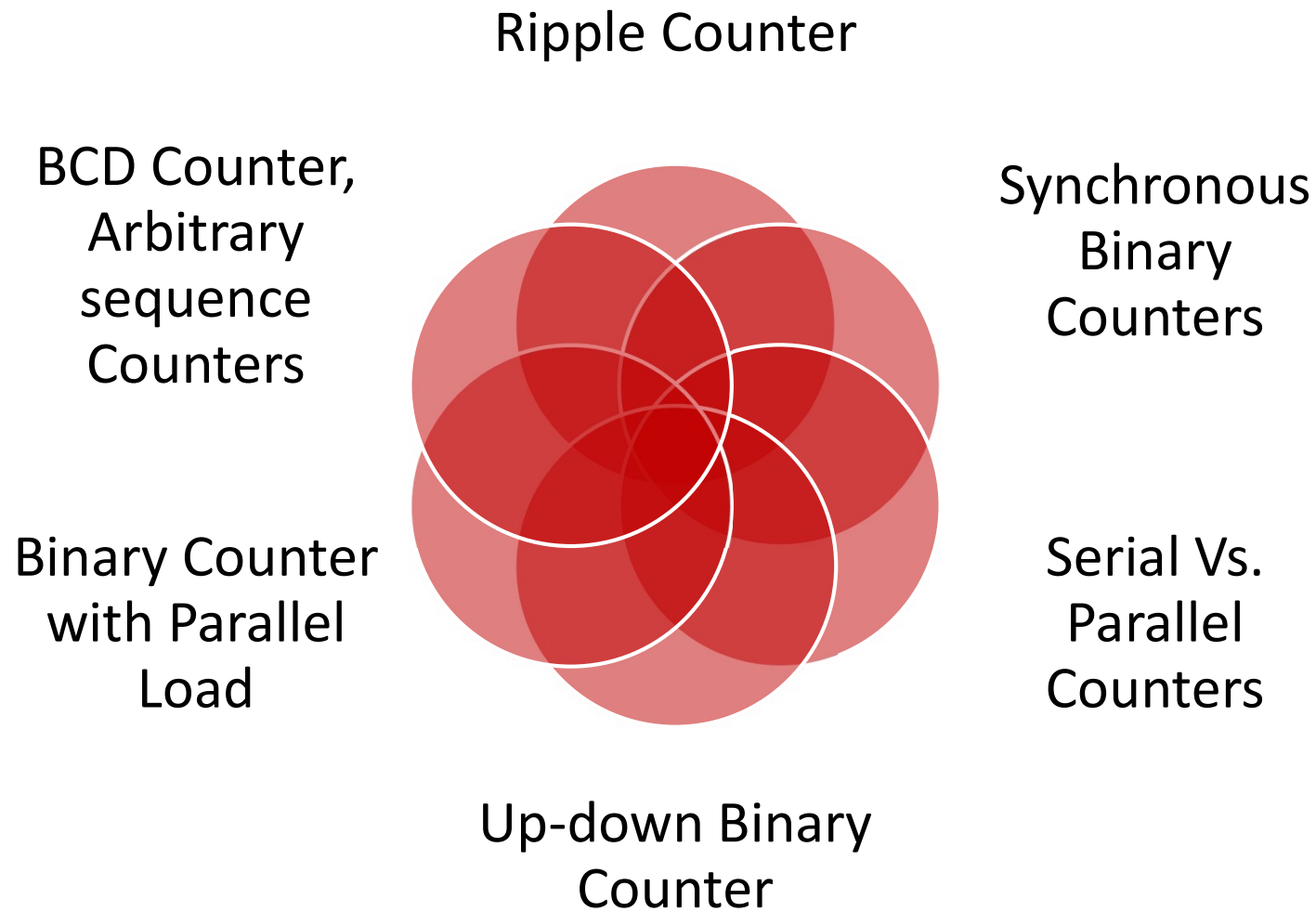


- A *counter* is a register that goes through a predetermined sequence of states upon the application of clock pulses.
- Counters are categorized as:
 - Ripple Counters:
The FF output transition serves as a source for triggering other FFs. No common clock.
 - Synchronous Counter:
All FFs receive the common clock pulse, and the change of state is determined from the present state.

Example: A 4-bit Upward Counting Ripple Counter

**Less Significant Bit output is Clock
for Next Significant Bit!
(Clock is active low)**

(a) JK Flip-Flop

J	K	$Q(t+1)$	Operation
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$\overline{Q}(t)$	Complement

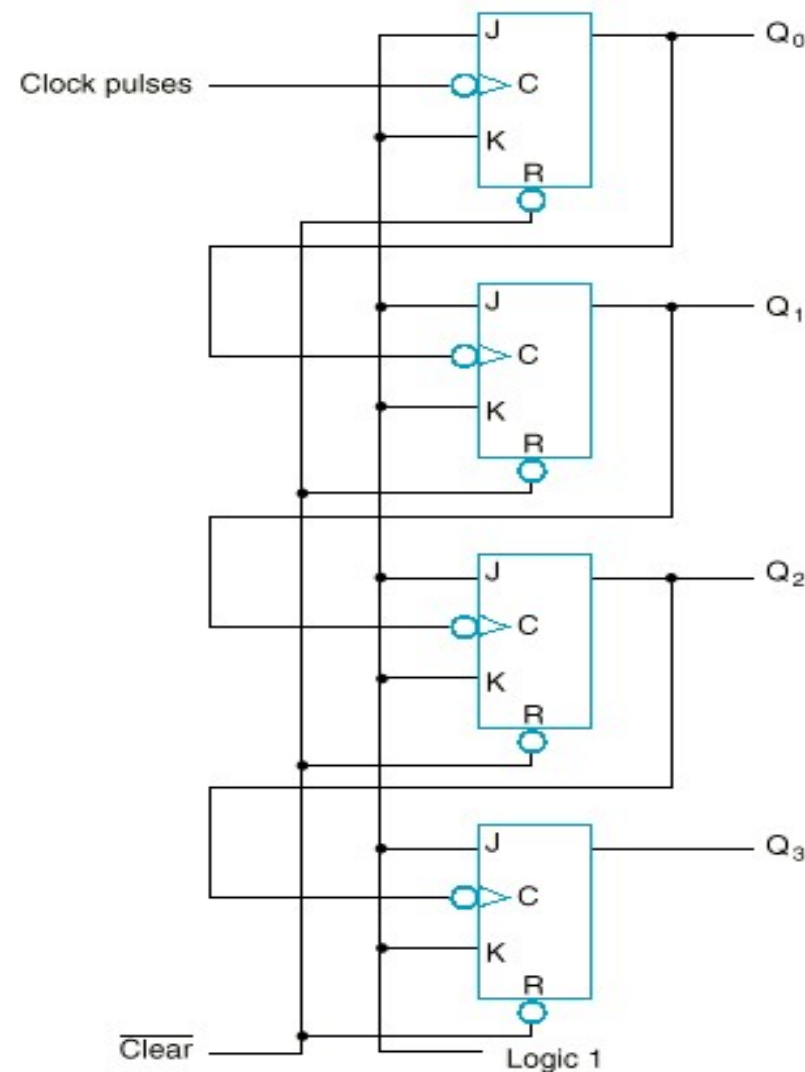



Example (cont.)

- The output of each FF is connected to the C input of the next FF in sequence.
- The FF holding the least significant bit receives the incoming clock pulses.
- The J and K inputs of all FFs are connected to a permanent logic 1.
- The bubble next to the C label indicates that the FFs respond to the negative-going transition of the input.

Example (cont.)

Operation:

- The least significant bit (Q_0) is complemented with each negative-edge clock pulse input.
- Every time that Q_0 goes from 1 to 0, Q_1 is complemented.
- Every time that Q_1 goes from 1 to 0, Q_2 is complemented.
- Every time that Q_2 goes from 1 to 0, Q_3 is complemented, and so on.

Upward Counting Sequence

Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Synchronous Binary Counters

- The design procedure for a binary counter is the same as any other synchronous sequential circuit.
- The primary inputs of the circuit are the CLK and any control signals (EN, Load, etc).
- The primary outputs are the FF outputs (present state).
- Most efficient implementations usually use T-FFs or JK-FFs. We will examine JK and D flip-flop designs.

Synchronous Binary Counters

J-K Flip Flop Design of a 4-bit Binary Up Counter

Present state				Next state			
Q_3	Q_2	Q_1	Q_0	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	1
1	0	1	1	1	1	0	0
1	1	0	0	1	1	0	1
1	1	0	1	1	1	1	0
1	1	1	0	1	1	1	1
1	1	1	1	0	0	0	0

J-K flip-flop characteristic table and equation

Present		Next	
J	K	Q_t	Q_{t+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q_{t+1} = JQ_t' + K'Q_t$$


J-K flip-flop excitation table

Q_t	Q_{t+1}	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0


Synchronous Binary Counters

J-K Flip Flop Design of a Binary Up Counter (cont.)

Present state				Next state					
Q_3	Q_2	Q_1	Q_0	Q_3	Q_2	Q_1	Q_0	J_{Q3}	K_{Q3}
0	0	0	0	0	0	0	1	0	X
0	0	0	1	0	0	1	0	0	X
0	0	1	0	0	0	1	1	0	X
0	0	1	1	0	1	0	0	0	X
0	1	0	0	0	1	0	1	0	X
0	1	0	1	0	1	1	0	0	X
0	1	1	0	0	1	1	1	0	X
0	1	1	1	1	0	0	0	1	X
1	0	0	0	1	0	0	1	X	0
1	0	0	1	1	0	1	0	X	0
1	0	1	0	1	0	1	1	X	0
1	0	1	1	1	1	0	0	X	0
1	1	0	0	1	1	0	1	X	0
1	1	0	1	1	1	1	0	X	0
1	1	1	0	1	1	1	1	X	0
1	1	1	1	0	0	0	0	X	1

 

$$J_{Q3} = Q_0 Q_1 Q_2$$

 

$$K_{Q3} = Q_0 Q_1 Q_2$$

Synchronous Binary Counters

J-K Flip Flop Design of a Binary Up Counter (cont.)

Present state				Next state				Flip-flop	
Q_3	Q_2	Q_1	Q_0	Q_3	Q_2	Q_1	Q_0	J_{Q_2}	K_{Q_2}
0	0	0	0	0	0	0	1	0	X
0	0	0	1	0	0	1	0	0	X
0	0	1	0	0	0	1	1	0	X
0	0	1	1	0	1	0	0	1	X
0	1	0	0	0	1	0	1	X	0
0	1	0	1	0	1	1	0	X	0
0	1	1	0	0	1	1	1	X	0
0	1	1	1	1	0	0	0	X	1
1	0	0	0	1	0	0	1	0	X
1	0	0	1	1	0	1	0	0	X
1	0	1	0	1	0	1	1	0	X
1	0	1	1	1	1	0	0	1	X
1	1	0	0	1	1	0	1	X	0
1	1	0	1	1	1	1	0	X	0
1	1	1	0	1	1	1	1	X	0
1	1	1	1	0	0	0	0	X	1

		1	
X	X	X	X
X	X	X	X
		1	

$$J_{Q_2} = Q_0 Q_1$$

X	X	X	X
		1	
		1	
X	X	X	X

$$K_{Q_2} = Q_0 Q_1$$

Synchronous Binary Counters

J-K Flip Flop Design of a Binary Up Counter (cont.)

Present state				Next state				p inputs	
Q_3	Q_2	Q_1	Q_0	Q_3	Q_2	Q_1	Q_0	J_{Q1}	K_{Q1}
0	0	0	0	0	0	0	1	0	X
0	0	0	1	0	0	1	0	1	X
0	0	1	0	0	0	1	1	X	0
0	0	1	1	0	1	0	0	X	1
0	1	0	0	0	1	0	1	0	X
0	1	0	1	0	1	1	0	1	X
0	1	1	0	0	1	1	1	X	0
0	1	1	1	1	0	0	0	X	1
1	0	0	0	1	0	0	1	0	X
1	0	0	1	1	0	1	0	1	X
1	0	1	0	1	0	1	1	X	0
1	0	1	1	1	1	0	0	X	1
1	1	0	0	1	1	0	1	0	X
1	1	0	1	1	1	1	0	1	X
1	1	1	0	1	1	1	1	X	0
1	1	1	1	0	0	0	0	X	1

	1	X	X
	1	X	X
	1	X	X
	1	X	X


$$J_{Q1} = Q_0$$

X	X	1	
X	X	1	
X	X	1	
X	X	1	

$$K_{Q1} = Q_0$$


Synchronous Binary Counters

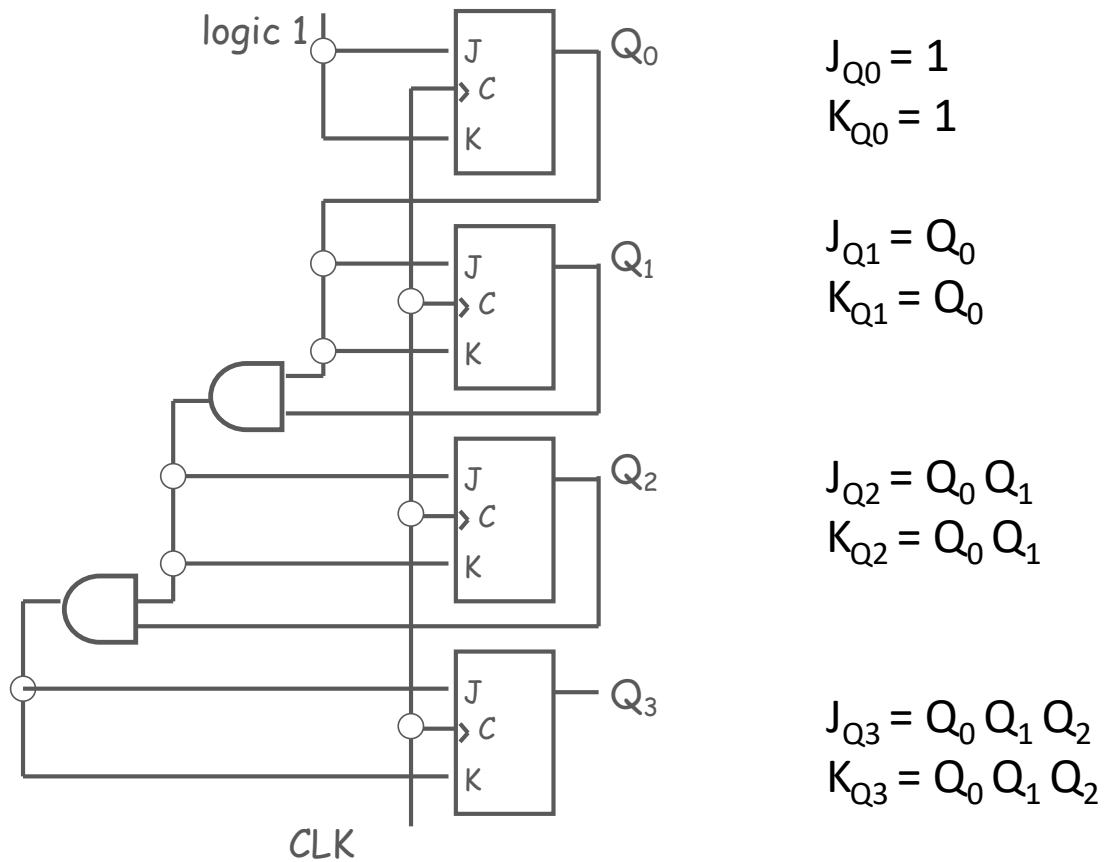J-K Flip Flop Design of a Binary Up Counter (cont.)



Synchronous Binary Counters

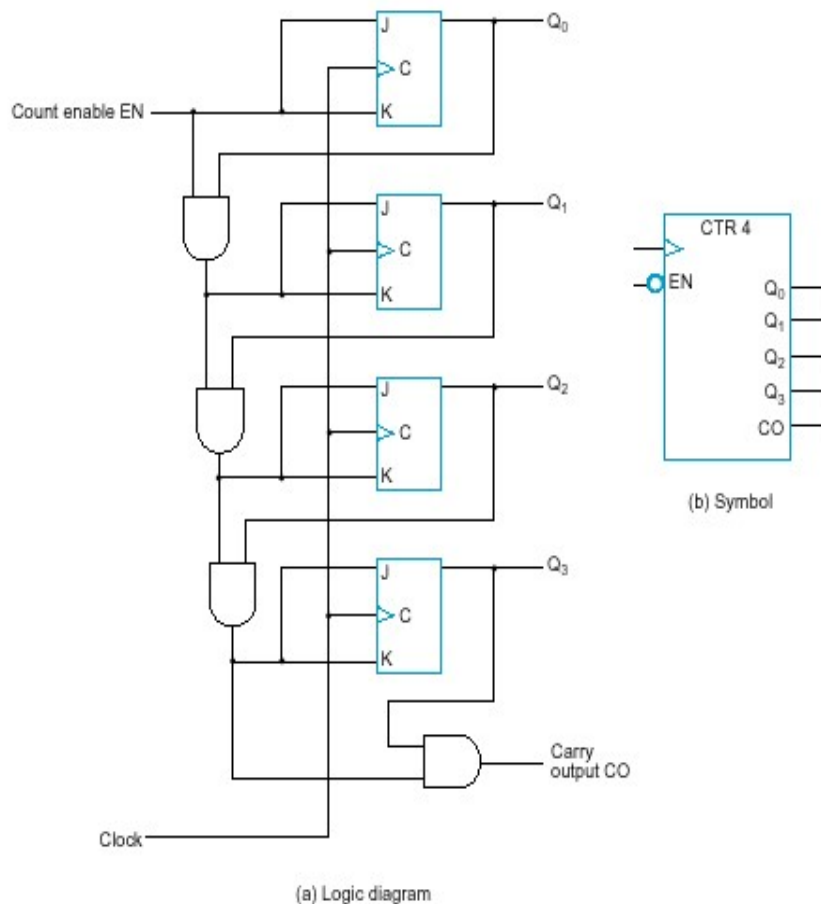J-K Flip Flop Design of a Binary Up Counter with EN and CO



EN = enable control signal, when 0 counter remains in the same state, when 1 it counts

CO = carry output signal, used to extend the counter to more stages

$$J_{Q0} = 1 \cdot EN$$

$$K_{Q0} = 1 \cdot EN$$

$$J_{Q1} = Q_0 \cdot EN$$

$$K_{Q1} = Q_0 \cdot EN$$

$$J_{Q2} = Q_0 Q_1 \cdot EN$$

$$K_{Q2} = Q_0 Q_1 \cdot EN$$

$$J_{Q3} = Q_0 Q_1 Q_2 \cdot EN$$

$$K_{Q3} = Q_0 Q_1 Q_2 \cdot EN$$

$$CO = Q_0 Q_1 Q_2 Q_3 \cdot EN$$

Synchronous Binary Counters using D flip-flops


- $D_{Q0} = Q_0 \oplus EN$
- $D_{Q1} = Q_1 \oplus (Q_0 \cdot EN)$
- $D_{Q2} = Q_2 \oplus (Q_0 Q_1 \cdot EN)$
- $D_{Q3} = Q_3 \oplus (Q_0 Q_1 Q_2 \cdot EN)$
- $CO = Q_0 Q_1 Q_2 Q_3 \cdot EN$

JK-FF equations

JK-based design calls for 4 AND gates

D-based design calls for 4 AND and 4 XOR gates

Up-Down Binary Counter

 

UD = 0: count up

UD = 1: count down



Up-Down Binary Counter (cont.)



四川大學
SICHUAN UNIVERSITY

UD	Q2	Q1	Q0	Q2.D	Q1.D	Q0.D	UD	Q2	Q1	Q0	Q2.D	Q1.D	Q0.D
0	0	0	0	0	0	1	1	0	0	0	1	1	1
0	0	0	1	0	1	0	1	0	0	1	0	0	0
0	0	1	0	0	1	1	1	0	1	0	0	0	1
0	0	1	1	1	0	0	1	0	1	1	0	1	0
0	1	0	0	1	0	1	1	1	0	0	0	1	1
0	1	0	1	1	1	0	1	1	0	1	1	0	0
0	1	1	0	1	1	1	1	1	1	0	1	0	1
0	1	1	1	0	0	0	1	1	1	1	1	1	0
Up-Counter							Down-Counter						

Finish the design in class



Binary Counter with Parallel Load

- (Next slide) gives the logic diagram and symbol of a 4-bit synchronous binary counter with parallel load capability. The function table for this binary counter is


Load	Count	Operation
0	0	Nothing
0	1	Count
1	x	Load



Binary Counter with Parallel Load




四川大學
SICHUAN UNIVERSITY

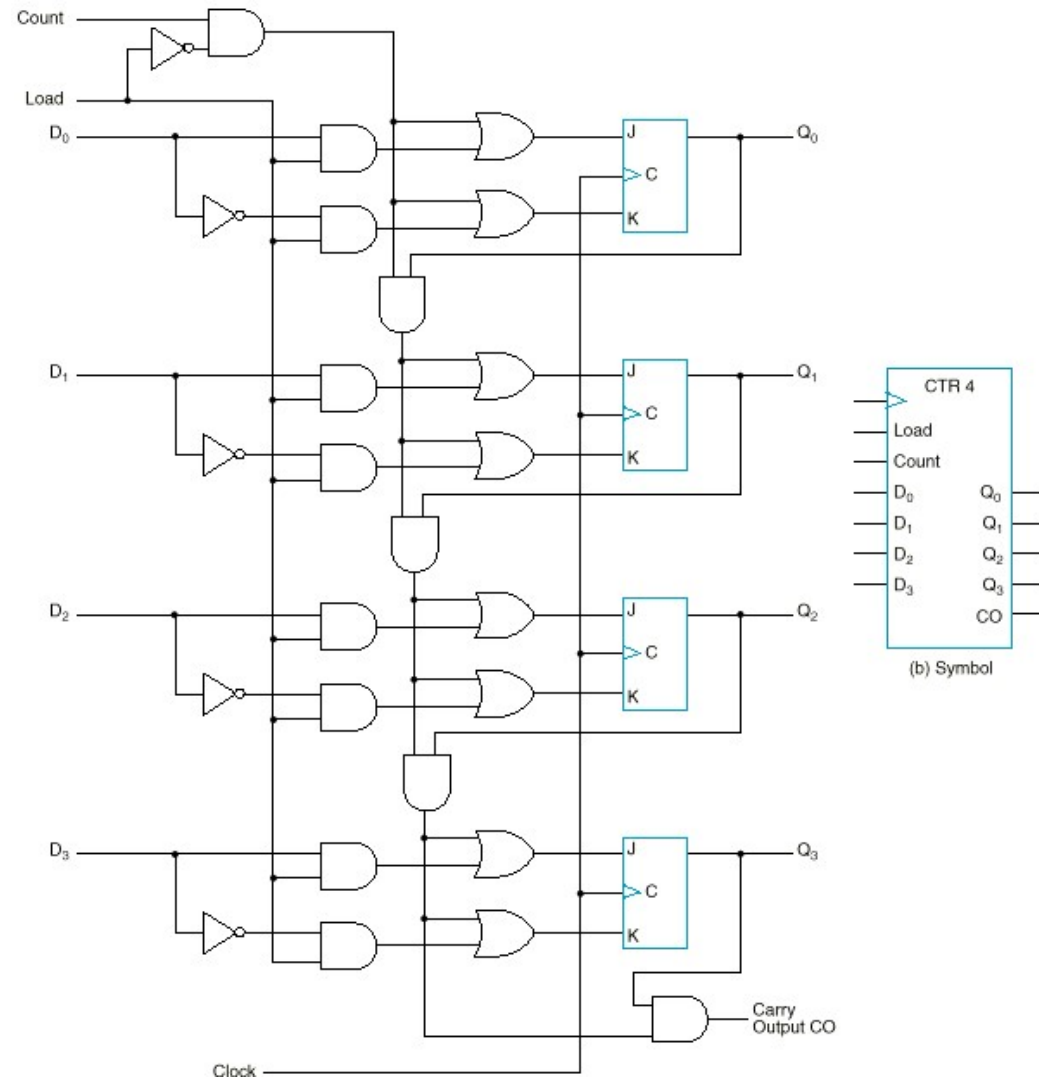

BCD counter

- The binary counter with parallel load can be converted into a synchronous BCD counter by connecting an external AND gate to it.

Load	Count	Operation
0	0	Nothing
0	1	Count
1	x	Load

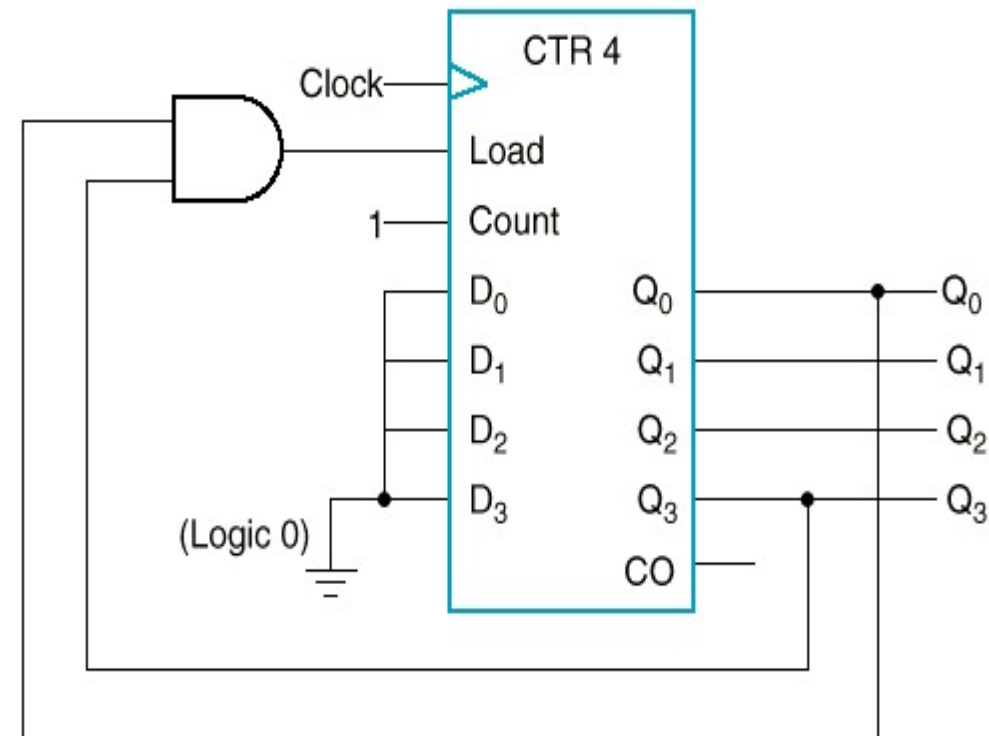

BCD counter (cont.)

- The counter starts with an all-zero output.
- As long as the output of the AND gate is 0, each positive clock pulse transition increments the counter by one.
- When the output reaches the count of 1001, both Q_0 and Q_3 become 1, making the output of the AND gate equal to 1. This condition makes Load active, so on the next clock transition, the counter does not count, but is loaded from its four inputs.
- The value loaded then is 0000.

Arbitrary Sequence Counter

- Given an arbitrary sequence, design a counter that will generate this sequence.
- Procedure:
 - Derive state table/diagram based on give sequence
 - Simplify (using K-maps, etc)
 - Draw logic diagram
- Example: Use D-FFs to draw the logic diagram for sequence generator (counter) for: $0 \rightarrow 7 \rightarrow 6 \rightarrow 1 \rightarrow 0$
($000 \rightarrow 111 \rightarrow 110 \rightarrow 001 \rightarrow 000$)

Example

- Use D-FFs to draw the logic diagram for sequence generator (counter) for: $0 \rightarrow 7 \rightarrow 6 \rightarrow 1 \rightarrow 0$ ($000 \rightarrow 111 \rightarrow 110 \rightarrow 001 \rightarrow 000$)

$Q_3Q_2Q_1$	$Q_3+Q_2+Q_1+$	$D_3D_2D_1$	Z
000	111	111	0
001	000	000	1
010	ddd	ddd	d
011	ddd	ddd	d
100	ddd	ddd	d
101	ddd	ddd	d
110	001	001	0
111	110	110	0

Example

Q_3Q_2		Q_1			
	Q_1	00	01	11	10
	0	1	d		d
	1		d	1	d

D₃ K-Map

Q_3Q_2		Q_1			
	Q_1	00	01	11	10
	0	1	d		d
	1		d	1	d

D₂ K-Map

Q_3Q_2		Q_1			
	Q_1	00	01	11	10
	0	1	d	1	d
	1		d		d

D₁ K-Map

Q_3Q_2		Q_1			
	Q_1	00	01	11	10
	0		d		d
	1	1	d		d

Z K-Map

$$D_3 = Q_3'Q_1' + Q_3Q_1$$

$$D_2 = Q_3'Q_1' + Q_3Q_1$$

$$D_1 = Q_1'$$

$$Z = Q_3'Q_1$$

$Q_3Q_2Q_1$	$Q_3+Q_2+Q_1+$	$D_3D_2D_1$	Z
000	111	111	0
001	000	000	1
010	ddd	ddd	d
011	ddd	ddd	d
100	ddd	ddd	d
101	ddd	ddd	d
110	001	001	0
111	110	110	0

Example


$$D_3 = Q_3'Q_1' + Q_3Q_1$$

$$D_2 = Q_3'Q_1' + Q_3Q_1$$

$$D_1 = Q_1'$$

$$Z = Q_3'Q_1$$

$Q_3Q_2Q_1$	$Q_3+Q_2+Q_1+$
010	111
011	000
100	001
101	110

 


Example

$$D_3 = Q_3'Q_1' + Q_3Q_1$$

$$D_2 = Q_3'Q_1' + Q_3Q_1$$

$$D_1 = Q_1'$$

$$Z = Q_3'Q_1$$

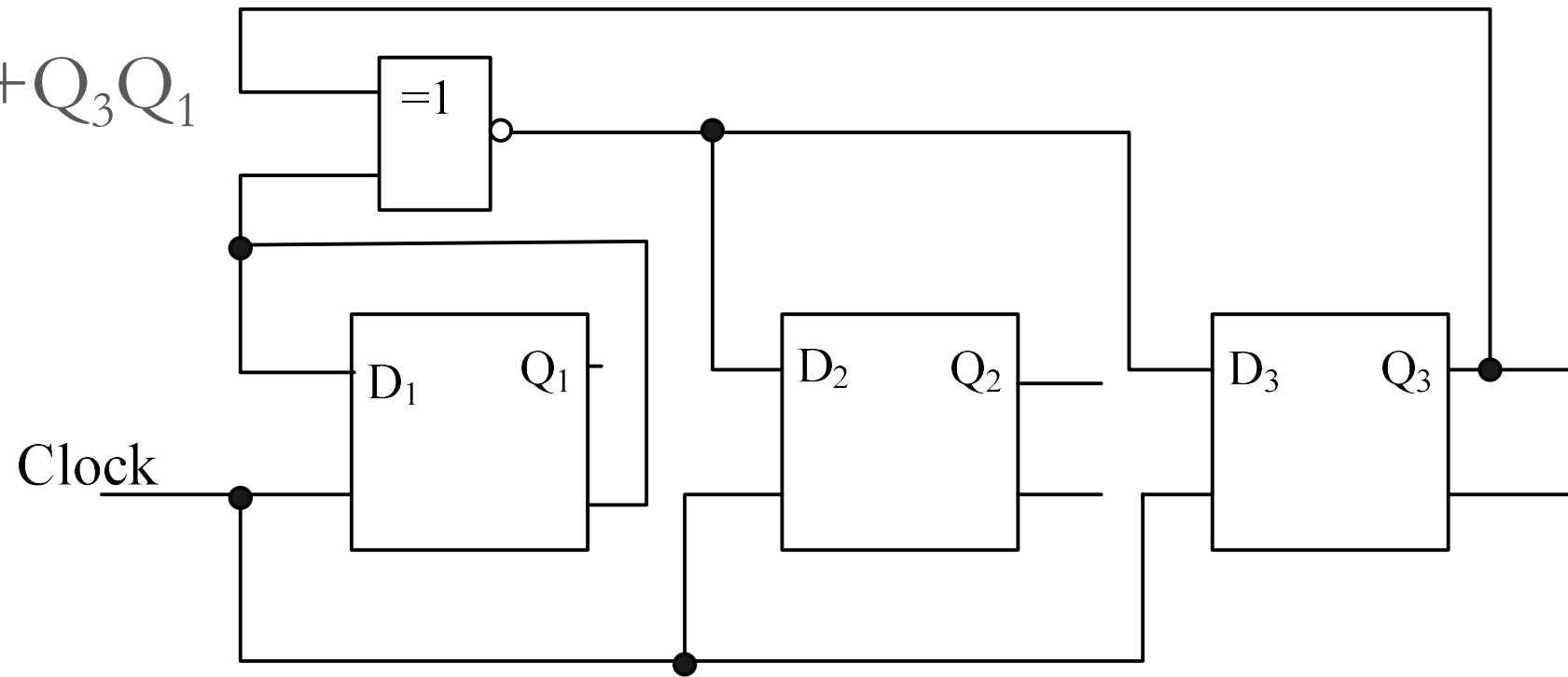

Homework

Thanks