



DIGITAL LOGIC

数字逻辑



Synchronous Sequential Circuit Analysis




- Analysis Principles
 - 1. Determine the system variables: input, state, and output.
 - 2. Determine the flip-flop type. Write the characteristic equations.
 - 3. write the excitation equations.
 - 4. write the next state equations.
 - 5. Write the output variable equations.
 - 6. Construct a transition table.
 - 7. Assign symbols to the states and construct a table or state diagram.
 - 8. When possible, construct a timing diagram.
 - 9. Functionality analysis



Analysis Examples



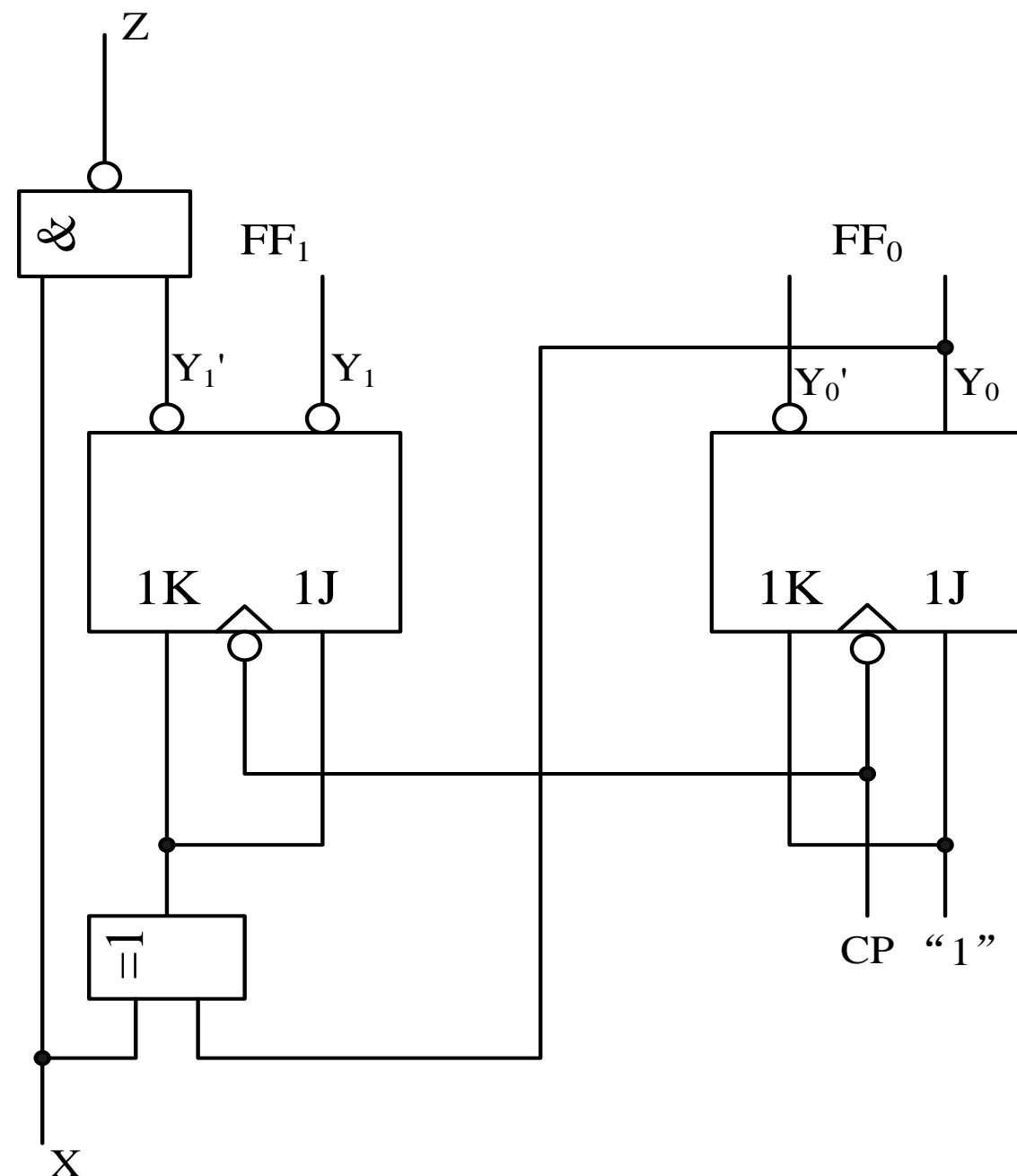- E.g.1: Analysis the following synchronous sequential circuit, suppose the present state is 00, the input sequence is 0000011111, give the timing diagram.





Analysis Examples

- 1. Determine the system variables: input, state, and output.

input= x

output= Z

state variables= y_1 and y_0


- 2. Determine the flip-flop type. Write the characteristic equations.

$$y^{n+1} = Jy^{n'} + k'y^n$$

- 3. write the excitation equations.

$$K_0 = J_0 = 1$$

$$K_1 = J_1 = x \oplus y_0$$

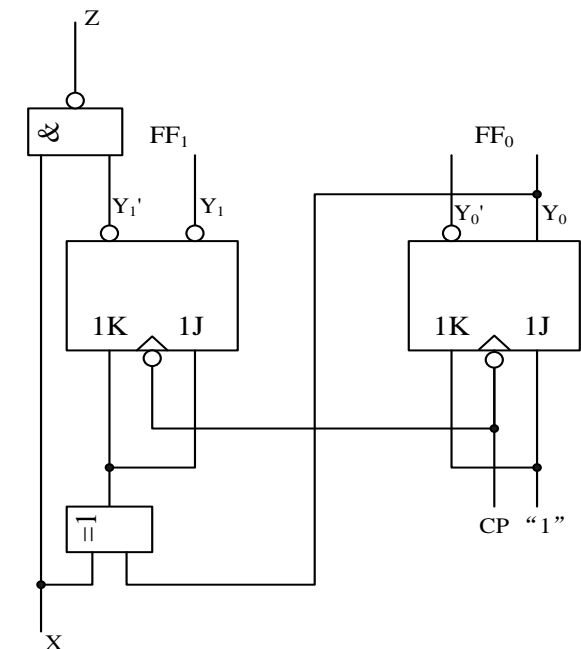



Analysis Examples


–4. write the next state equations.

$$\left. \begin{aligned} y_1^{n+1} &= J_1 y_1' + k_1' y_1 \\ y_0^{n+1} &= J_0 y_0' + k_0' y_0 \end{aligned} \right\} \longrightarrow \left\{ \begin{aligned} y_1^{n+1} &= x' y_1' y_0 + x' y_1 y_0' + x y_1' y_0' + x y_1 y_0 \\ y_0^{n+1} &= y_0' \end{aligned} \right.$$

–5. Write the output variable equations.

$$Z = (x y_1')' = x' + y_1$$

–6. Construct a transition table.

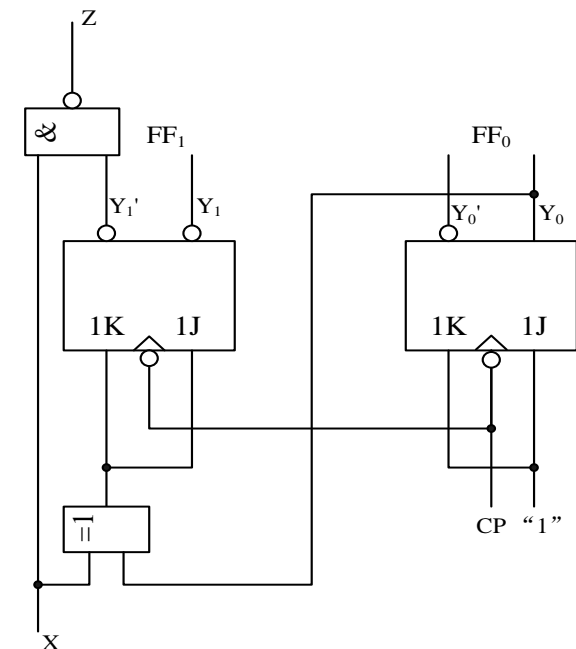



Analysis Examples



四川大学
SICHUAN UNIVERSITY

$$\begin{cases} y_1^{n+1} = x'y_1'y_0 + x'y_1y_0' + xy_1'y_0' + xy_1y_0 \\ y_0^{n+1} = y_0' \\ Z = (xy_1')' = x' + y_1 \end{cases}$$

Y ₁ Y ₀ \ X	0	1
	0	1
00	0	1
01	1	0
11	0	1
10	1	0

Y₁ⁿ⁺¹ K-Map

Y ₁ Y ₀ \ X	0	1
	0	1
00	1	1
01	0	0
11	0	0
10	1	1

Y₀ⁿ⁺¹ K-Map

Y ₁ Y ₀ \ X	0	1
	0	1
00	1	0
01	1	0
11	1	1
10	1	1

Z K-Map



Present state Y ₁ Y ₀	Next state x/z					
	X=0			X=1		
	Y ₁ +	Y ₀ +	/ Z	Y ₁ +	Y ₀ +	/ Z
00	0	1	1	1	1	0
01	1	0	1	0	0	0
11	0	0	1	1	0	1
10	1	1	1	0	1	1

transition table




Analysis Examples



- 7. Assign symbols to the states and construct a table or state diagram

	Present state $Y_0 \ Y_1$	Next state x/z	
		X=0	X=1
		$Y_{0+} \ Y_{1+} / Z$	$Y_{0+} \ Y_{1+} / Z$
Q_1	00	01/1	11/0
Q_2	01	10/1	00/0
Q_4	11	00/1	10/1
Q_3	10	11/1	01/1


Present state $Y_0 \ Y_1$	Next state x/z	
	X=0	X=1
	$Y_{0+} \ Y_{1+} / Z$	$Y_{0+} \ Y_{1+} / Z$
Q_1	$Q_2/1$	$Q_4/0$
Q_2	$Q_3/1$	$Q_1/0$
Q_3	$Q_4/1$	$Q_2/1$
Q_4	$Q_1/1$	$Q_3/1$

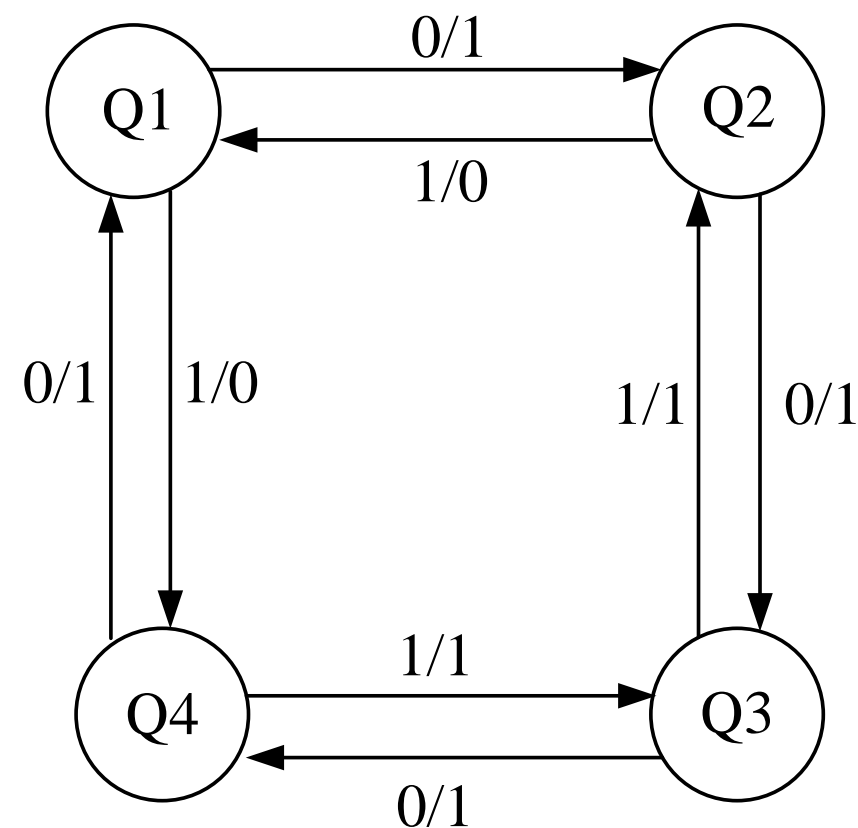



Analysis Examples

– 8. construct a timing diagram.

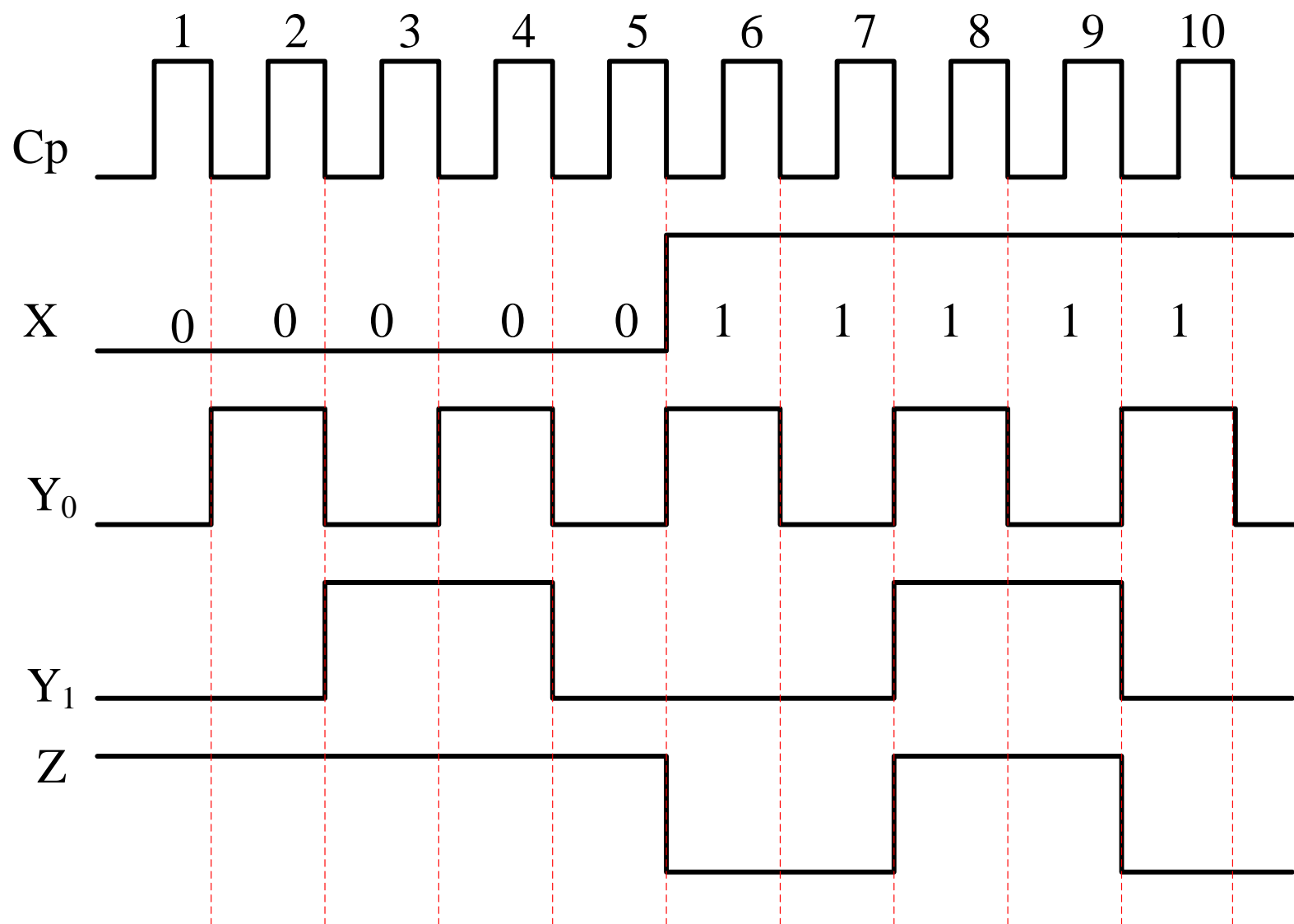


$$\begin{cases} y_1^{n+1} = x'y_1'y_0 + x'y_1y_0' \\ \quad + xy_1'y_0' + xy_1y_0 \\ y_0^{n+1} = y_0' \\ Z = (xy_1')' = x' + y_1 \end{cases}$$



Analysis Examples



- E.g.2: Analysis the following circuit

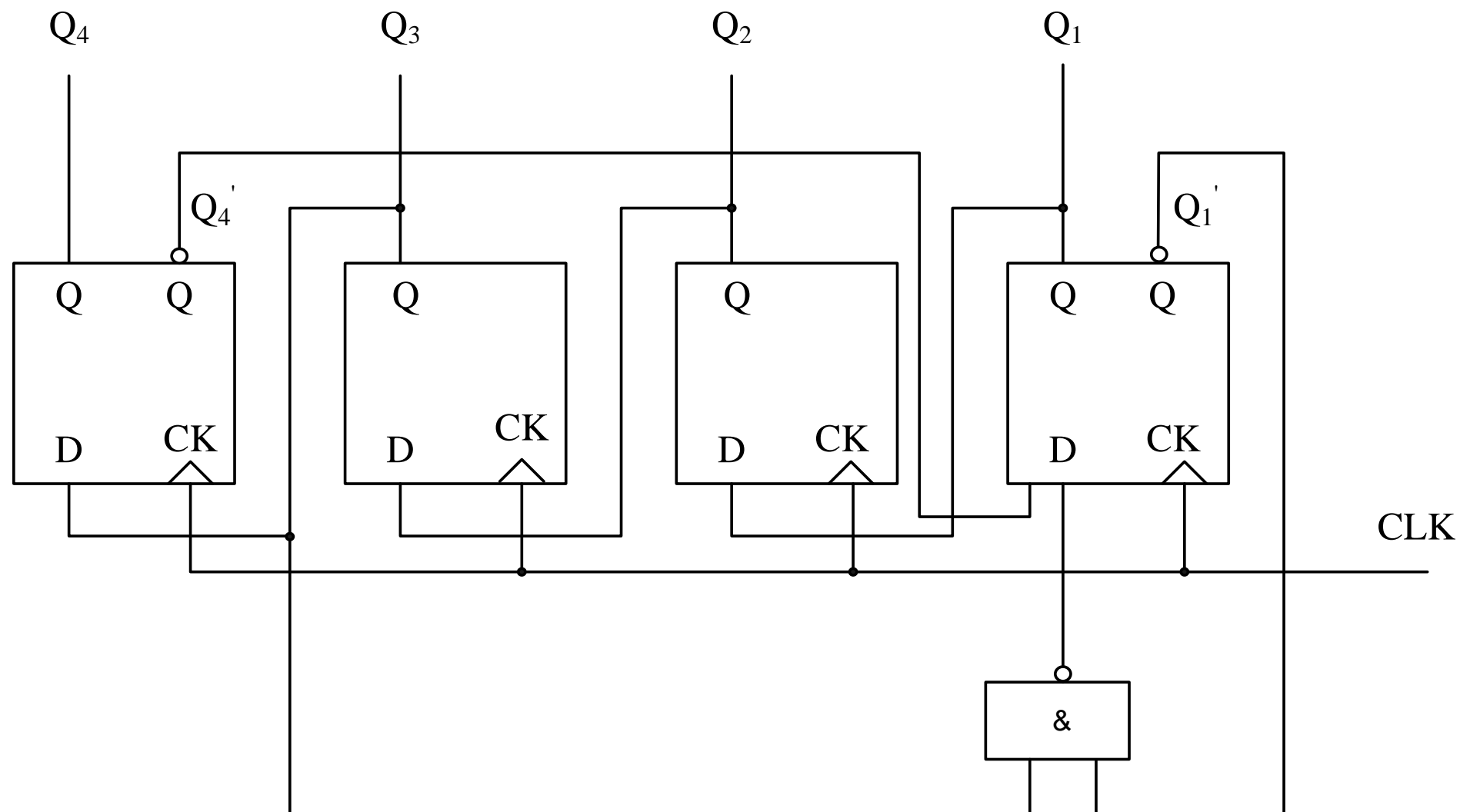



Analysis Examples

- 1. Determine the system variables: input, state, and output.

state variables: Q_1, Q_2, Q_3 , and Q_4

- 2. Determine the flip-flop type. Write the characteristic equations.

$$Q^{n+1} = D$$


- 3. excitation equations.

$$D_4 = Q_3$$

$$D_3 = Q_2$$

$$D_2 = Q_1$$
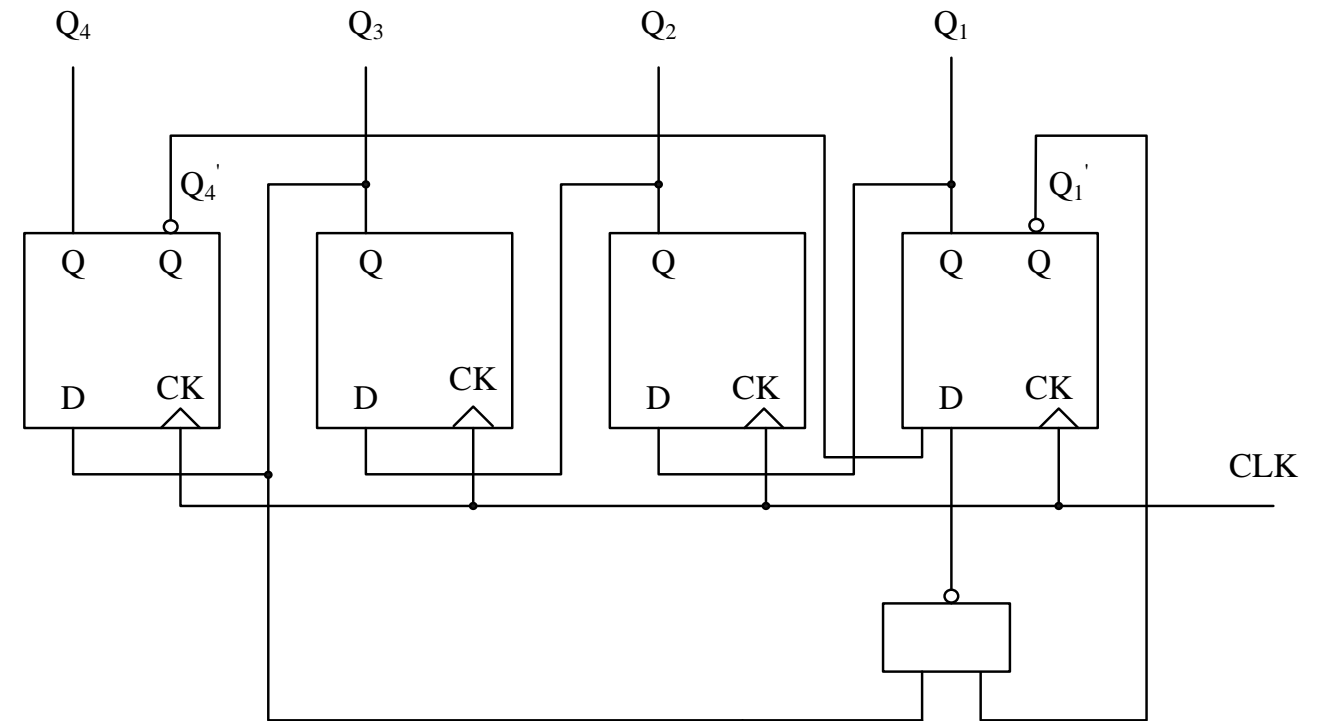
$$D_1 = Q_4'(Q_3Q_1')' = Q_4'Q_3' + Q_4'Q_1$$





Analysis Examples



– 4. the next state equations.

$$Q_4^{n+1} = Q_3$$

$$Q_3^{n+1} = Q_2$$

$$Q_2^{n+1} = Q_1$$

$$Q_1^{n+1} = Q_4'Q_3' + Q_4'Q_1$$

$$Q^{n+1} = D$$

$$D_4 = Q_3$$

$$D_3 = Q_2$$

$$D_2 = Q_1$$

$$D_1 = Q_4'(Q_3Q_1')' = Q_4'Q_3' + Q_4'Q_1$$



Analysis Examples



– 5. Construct a transition table.

$$Q_4^{n+1} = Q_3$$

$$Q_3^{n+1} = Q_2$$

$$Q_2^{n+1} = Q_1$$

$$Q_1^{n+1} = Q_4'Q_3' + Q_4'Q_1$$

Q_4	Q_3	Q_2	Q_1	Q_4^{n+1}	Q_3^{n+1}	Q_2^{n+1}	Q_1^{n+1}
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0




Analysis Examples



- 6. Assign symbols to the states and construct a table or state diagram.

Q_4 Q_3 Q_2 Q_1	S_0	S_1	S_2	S_3	S_4	S_5	S_6	S_7	S_8	S_9	S_{10}	S_{11}	S_{12}	S_{13}	S_{14}	S_{15}
$Q_4^{n+1} Q_3^{n+1} Q_2^{n+1} Q_1^{n+1}$	S_1	S_3	S_5	S_7	S_8	S_{11}	S_{12}	S_{15}	S_0	S_2	S_4	S_6	S_8	S_{10}	S_{12}	S_{14}

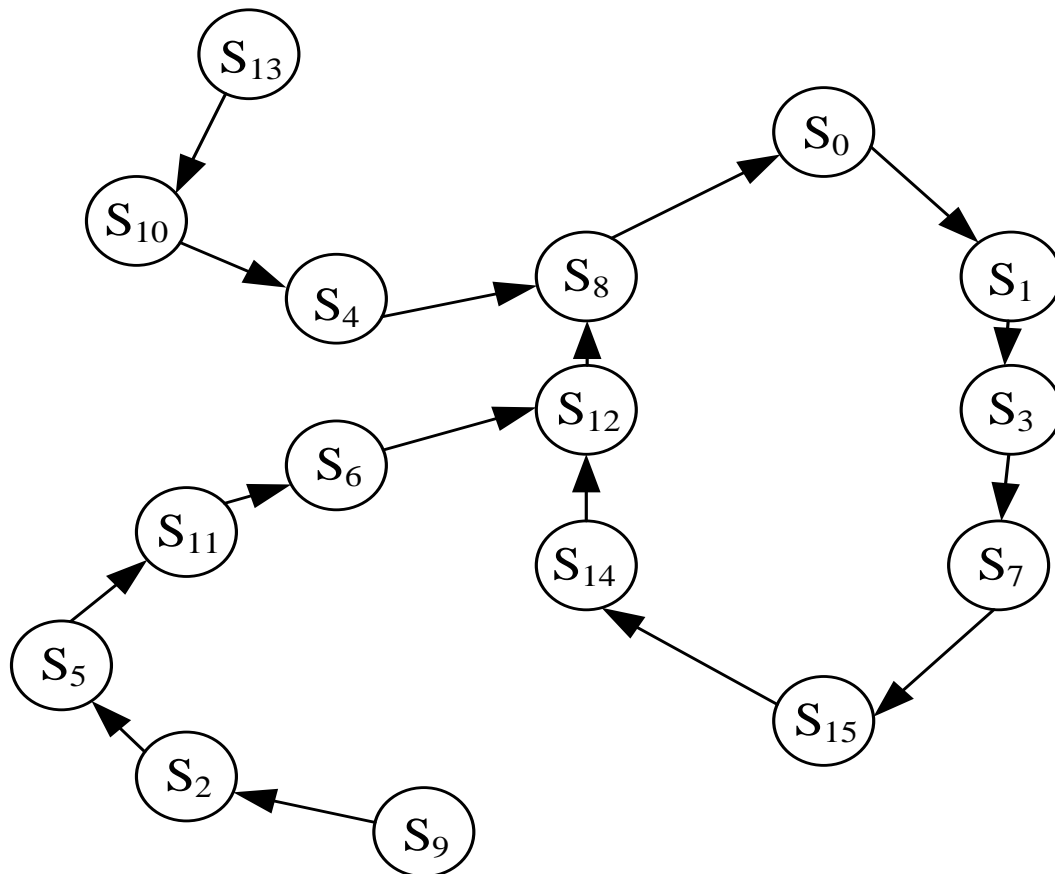


Q_4	Q_3	Q_2	Q_1	Q_4^{n+1}	Q_3^{n+1}	Q_2^{n+1}	Q_1^{n+1}
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	1
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	1	0
1	1	1	0	1	1	0	0
1	1	1	1	1	1	1	0



Analysis Examples



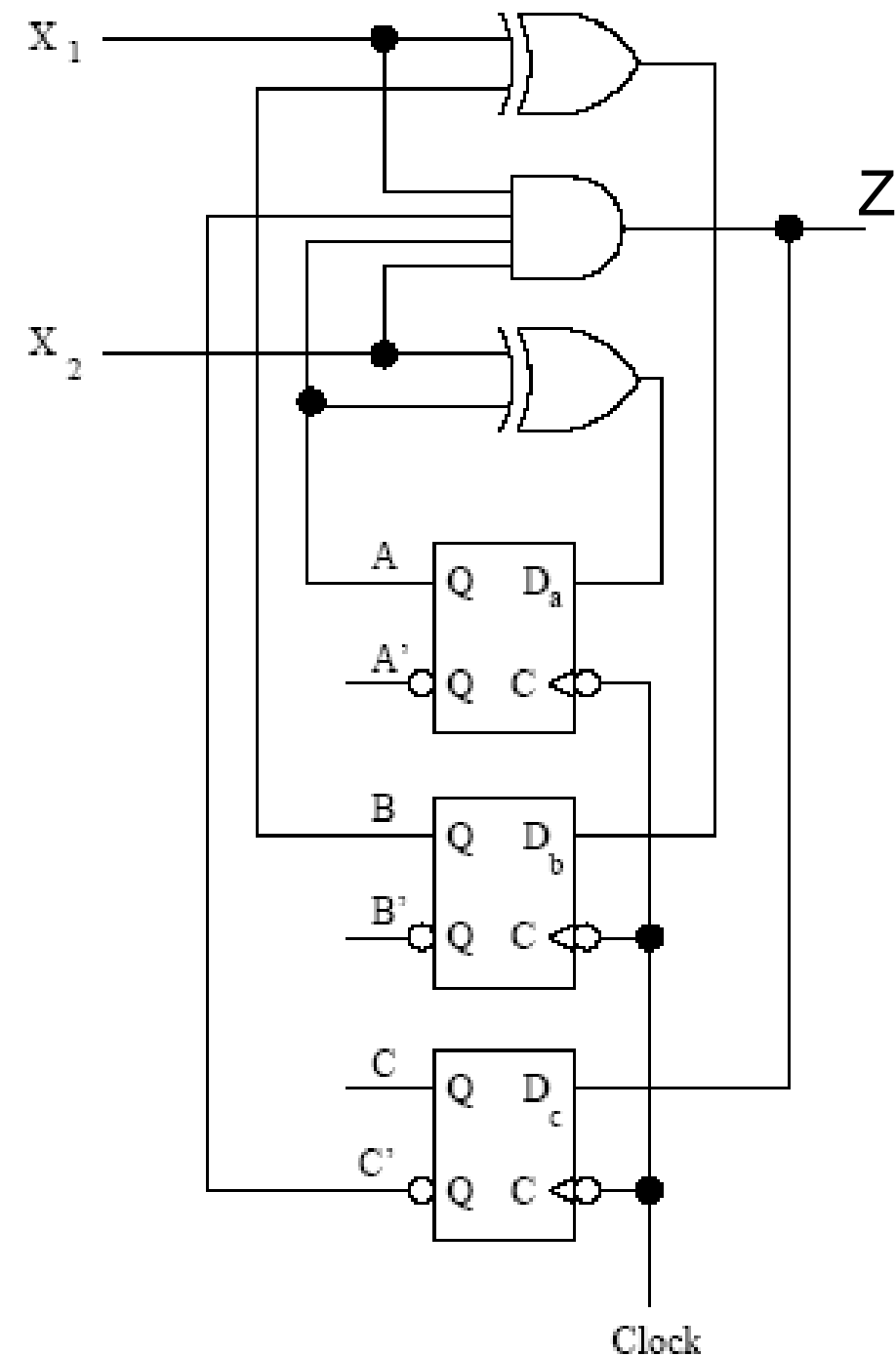- E.g.3: Find the transition table and the state table for the Mealy sequential circuit below.





Analysis Examples

- 1. Determine the system variables: input, state, and output.

input: x_1, x_2

output: Z

state variable: D_a, D_b, D_c

- 2. Determine the flip-flop type. Write the characteristic equations.

$$Q_{n+1} = D$$


- 3. Excitation equations and output equations.

$$D_a = Q_a \oplus X_2$$

$$D_b = Q_b \oplus X_1$$

$$D_c = X_1 X_2 Q_c' Q_a$$

$$Z = X_1 X_2 Q_c' Q_a$$

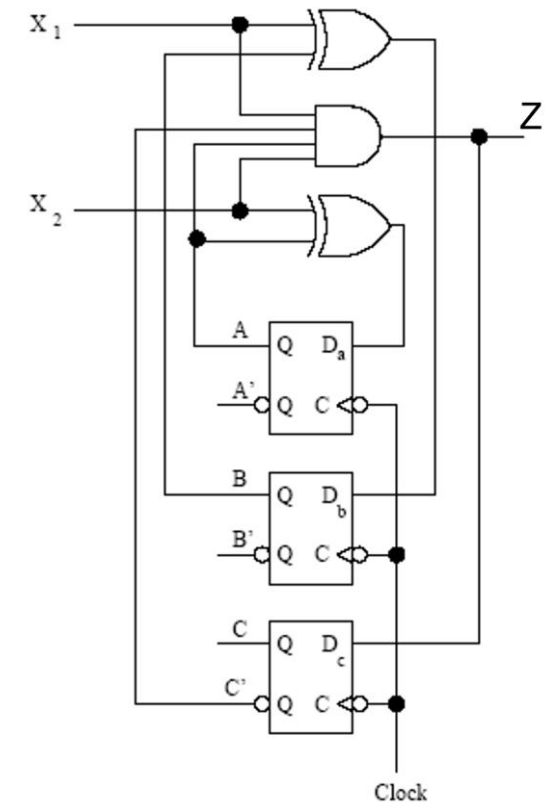



Analysis Examples



- 4. write the next state equations.

$$Q_a^{n+1} = Q_a X_2' + Q_a' X_2$$

$$Q_b^{n+1} = Q_b X_1' + Q_b' X_1$$

$$Q_c^{n+1} = X_1 X_2 Q_c' Q_a$$


- 5. Construct a transition table.

$$D_a = Q_a \oplus X_2$$

$$D_b = Q_b \oplus X_1$$

$$D_c = X_1 X_2 Q_c' Q_a$$

$$Z = X_1 X_2 Q_c' Q_a$$

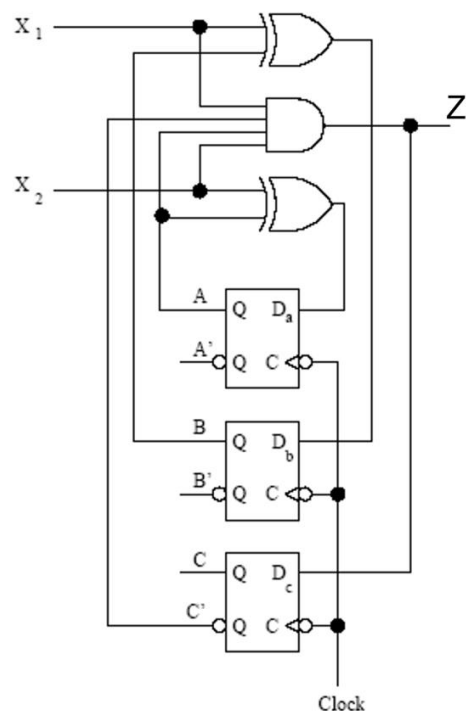

Q _a Q _b Q _c	X ₁ X ₂			
	Q _a + Q _b + Q _c +Z			
	X=00	X=01	X=10	X=11
000	000/0	100/0	010/0	110/0
001	000/0	100/0	010/0	110/0
010	010/0	110/0	000/0	100/0
011	010/0	110/0	000/0	100/0
100	100/0	000/0	110/0	011/1
101	100/0	000/0	110/0	010/0
110	110/0	010/0	100/0	001/1
111	110/0	010/0	100/0	000/0



– 6. Assign symbols to the states and construct a state table

$Q_a Q_b Q_c$	$Q_a+ Q_b+ Q_c+ /Z$				$Q_a Q_b Q_c$	$Q_a+ Q_b+ Q_c+ /Z$			
	X=00	X=01	X=10	X=11		X=00	X=01	X=10	X=11
000	000/0	100/0	010/0	110/0	A	A/0	E/0	C/0	G/0
001	000/0	100/0	010/0	110/0	B	A/0	E/0	C/0	G/0
010	010/0	110/0	000/0	100/0	C	C/0	G/0	A/0	E/0
011	010/0	110/0	000/0	100/0	D	C/0	G/0	A/0	E/0
100	100/0	000/0	110/0	011/1	E	E/0	A/0	G/0	D/1
101	100/0	000/0	110/0	010/0	F	E/0	A/0	G/0	C/0
110	110/0	010/0	100/0	001/1	G	G/0	C/0	E/0	B/1
111	110/0	010/0	100/0	000/0	H	G/0	C/0	E/0	A/0



Homework



四川大學
SICHUAN UNIVERSITY

Thanks